4-bit LED counter from logic gates

Four LEDs, one per bit, driven by AND, OR and NOT gates on a breadboard to show a set sequence of numbers on repeat.

digital-logic breadboard Oct 2026

Author	Sao Aphisith Sithisack	Date	October 13, 2026
Tools	Logic gates	Bits	4 LEDs
Logic	AND / OR / NOT	Online	https://saosith.github.io/projects/led-4bit-counter/

Built. Built on a breadboard and working. No measurements are recorded on this page.

What it does

Each of the four LEDs is one bit of a binary number. I wired AND, OR and NOT gates so the LEDs step through a set sequence of numbers and then repeat.

Details to add

Not yet **The gate chips used, the number sequence, and how the clock is generated.** Add these before publishing.